
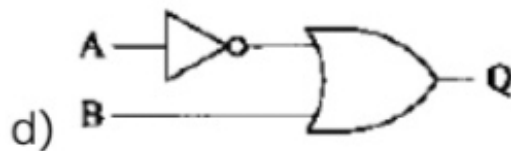
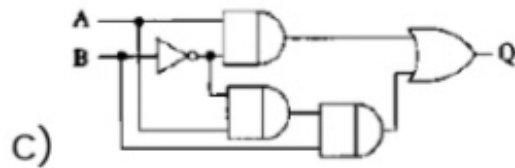
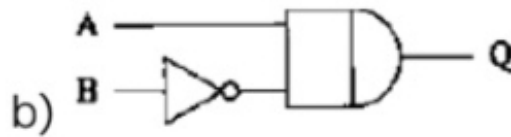


Name: Srinidhi A
ID: COMETFWC053

GATE Question No. 41

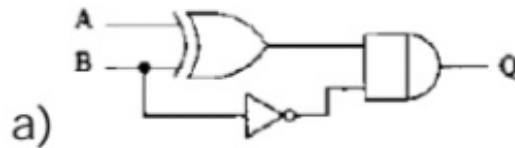Question:

For any set of inputs, A and B , the following circuits give the same output, Q , except one. Identify which one is different.



(GATE PH 2010)

Solution

We simplify each circuit using Boolean algebra.

Step 1: Circuit (a)

From the diagram, output is AND of $(A + B)$ and B' .

$$Q_a = (A + B) \cdot B'$$

Using distributive law:

$$Q_a = AB' + BB'$$

Since $BB' = 0$,

$$Q_a = AB'$$

Step 2: Circuit (b)

$$Q_b = AB'$$

Step 3: Circuit (c)

After simplifying internal gates,

$$Q_c = AB'$$

Step 4: Circuit (d)

$$Q_d = A' + B$$

Truth Table:

A	B	AB'	$A' + B$
0	0	0	1
0	1	0	1
1	0	1	0
1	1	0	1

Circuits (a), (b), and (c) give same output.

Circuit (d) gives different output.

Correct Answer: Option (d)